

Physics 313 assignment 5 for Thursday, October 2, 2018:

Topics: transistors

Reading: my notes, supplementary info on transistors (see website)

General questions

1. For the transistor whose characteristic curves are shown at right,

- Roughly what is the value of β (or h_{FE}) at V_{CE} of 4 volts, say.
- If the power rating of the transistor P_{max} is 0.05 W, is there any region of the curves shown for which P_{max} would be exceeded? (Power dissipated by a BJT $\sim V_{CE}I_C$.) Explain. Also, shade in roughly the region where P_{max} is exceeded.

2. For the common-emitter amplifier,

- Is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?

3. For the emitter follower (a.k.a. common collector),

- is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?

Problems: (assume that all transistors are npn silicon, like the 2N3904)

4) This is an emitter follower with the base biased quiescently above ground so that a single supply can be used without clipping negative input signals.

- Find the expected quiescent values of V_B , V_E , and V_C .
- Find the expected quiescent values of I_B , I_E , and I_C (hint: start with I_E and assume $\beta=100$).
- Check to make sure that the quiescent I_B is small compared to the quiescent current through the 50k resistor. Why is it important to design the circuit so that this is the case?
- For roughly what range of V_{in} (+ and -) is the output free from clipping?
- Would you need the 45k and 50k resistors if you had a $-15V$ power supply as well as a $+15V$ supply available? Why?

