

Physics 313 assignment 5 for Tuesday, September 27:

Topics: transistors

Reading questions:

1. For the transistor whose characteristic curves are shown at right,

a) Roughly what is the value of β (or h_{FE}) at V_{CE} of 4 volts, say.

b) If the power rating of the transistor P_{max} is 0.05 W, is there any region of the curves shown for which P_{max} would be exceeded? (Power dissipated by a BJT $\sim V_{CE}I_C$.) Explain. Also, shade in roughly the region where P_{max} is exceeded.

2. Setting a voltage at the base of a transistor that's high enough that the base current will be greater than zero for all expected signals is called setting the quiescent point (or "operating point"). What does the word quiescent mean? Give your source. (If you find several definitions, give the one that seems most closely related to its use in this context.)

3. What do the small v 's and i 's used in the textbook mean as distinct from the capital V 's and I 's? (Hint: go back to the first chapter on AC circuits).


4. For the common-emitter amplifier,

- Is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?
- What is the expression for the input impedance?
- What is the expression for the output impedance?

5. For the emitter follower (a.k.a. common collector),

- Is there voltage gain (that is, is v_{out}/v_{in} different from 1)? If so, what does the gain depend on?
- What is the expression for the input impedance? Is this typically a big or a small number?
- What is the expression for the output impedance? Is this typically a big or a small number?

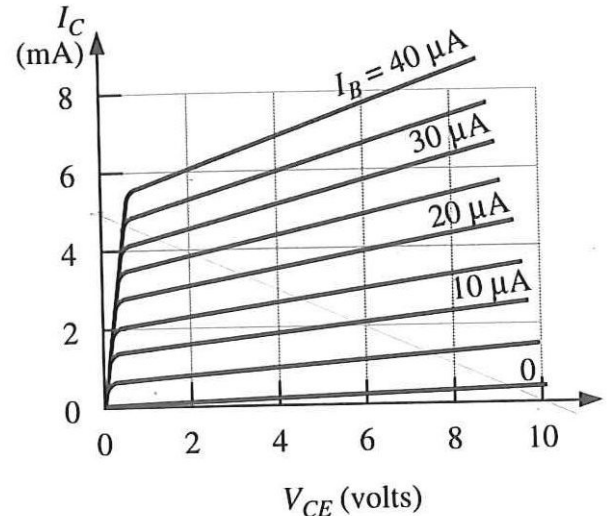
6. Why is it usually useful for a circuit to have a high input impedance and a low output impedance?




Problems: (assume that all transistors are npn silicon, like the 2N3904)

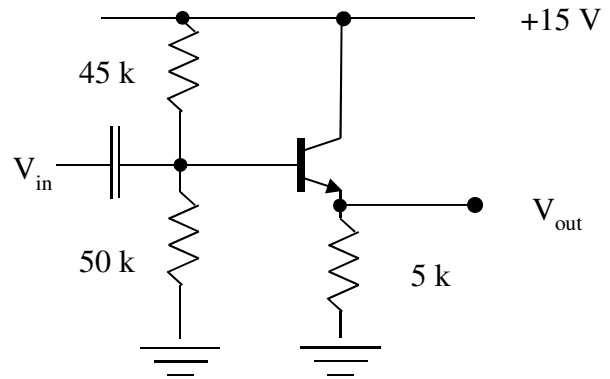1) This is an emitter follower with the base biased quiescently above ground so that a single supply can be used without clipping negative input signals.


- Find the expected quiescent values of V_B , V_E , and V_C .
- Find the expected quiescent values of I_B , I_E , and I_C (hint: start with I_E and assume $\beta=100$).
- Check to make sure that the quiescent I_B is small compared to the quiescent current through the 50k resistor. Why is it important to design the circuit so that this is the case?
- For roughly what range of V_{in} (+ and -) is the output free from clipping?
- Would you need the 45k and 50k resistors if you had a -15V power supply as well as a +15V supply available? Why?



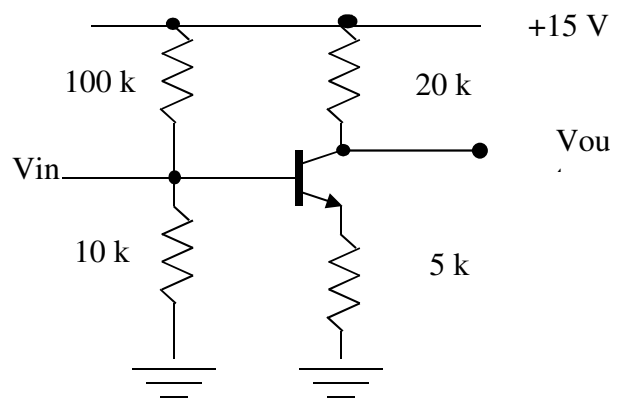- For the common-emitter amplifier at right, what do you expect the quiescent values of V_B , V_E , V_C , I_B , I_E , and I_C to be?
- What are R_{in} , R_{out} , and the voltage gain for the circuit above?
- What is the quiescent value of V_{CE} ? Is this value in the range for which we expect the current gain to be the full $\beta \sim 100$? Explain briefly.



- For the common-emitter amplifier in at right, with $V_{CC}=+15$ V,
 - Choose values for R_C , R_E , R_1 , and R_2 given that the magnitude of the desired voltage amplification is 10, the output resistance should be 10 k, and the quiescent V_{out} should be +6 V. Make sure the 10x rule is obeyed by the transistor and the voltage divider used to bias the base. That is, the transistor (and what follows it) should have a significantly higher impedance than the voltage divider, so that the transistor presents a small "load" to the voltage divider. This implies that the Thévenin resistance of the voltage divider should be at least 10 times smaller than βR_E .
 - Choose the value of C_1 to pass input signals with frequencies above about 500 Hz. Hint: You can treat the circuit as an RC high-pass filter with C_1 as the capacitor and $R_{in}=R_1||R_2||\beta R_E$ as the resistor.

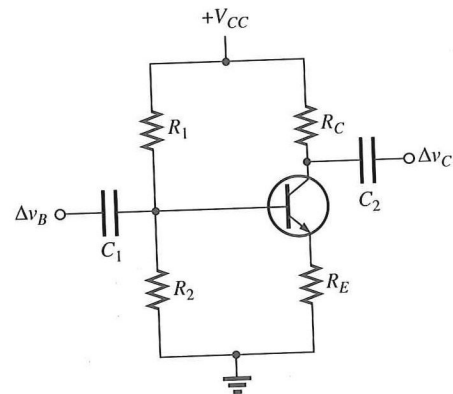

- For a 0.5 V amplitude input sine wave at 10 kHz, give the expected amplitude and frequency of the output signal. Explain briefly. Is the output signal inverted? Is the output signal offset from ground, and if so, by how much?
- What happens if the input signal is a 1.0 V amplitude input sine wave at 10 kHz? Explain your reasoning.

Physics 313 assignment 5 for Tuesday, September 27:

Topics: transistors


Reading questions:

1. For the transistor whose characteristic curves are shown at right,

a) Roughly what is the value of β (or h_{FE}) at V_{CE} of 4 volts, say.

b) If the power rating of the transistor P_{max} is 0.05 W, is there any region of the curves shown for which P_{max} would be exceeded? (Power dissipated by a BJT $\sim V_{CE}I_C$.) Explain. Also, shade in roughly the region where P_{max} is exceeded.

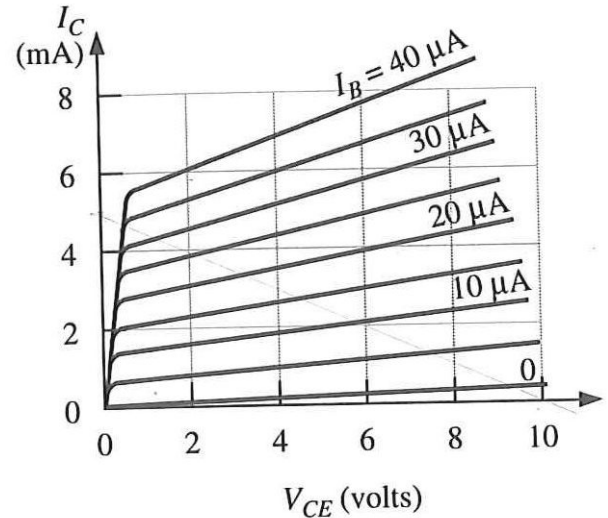2. Setting a voltage at the base of a transistor that's high enough that the base current will be greater than zero for all expected signals is called setting the quiescent point (or "operating point"). What does the word quiescent mean? Give your source. (If you find several definitions, give the one that seems most closely related to its use in this context.)



3. What do the small v 's and i 's used in the textbook mean as distinct from the capital V 's and I 's? (Hint: go back to the first chapter on AC circuits).

4. For the common-emitter amplifier,

- Is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?
- What is the expression for the input impedance?
- What is the expression for the output impedance?

5. For the emitter follower (a.k.a. common collector),


- Is there voltage gain (that is, is v_{out}/v_{in} different from 1)? If so, what does the gain depend on?
- What is the expression for the input impedance? Is this typically a big or a small number?
- What is the expression for the output impedance? Is this typically a big or a small number?

6. Why is it usually useful for a circuit to have a high input impedance and a low output impedance?


Problems: (assume that all transistors are npn silicon, like the 2N3904)

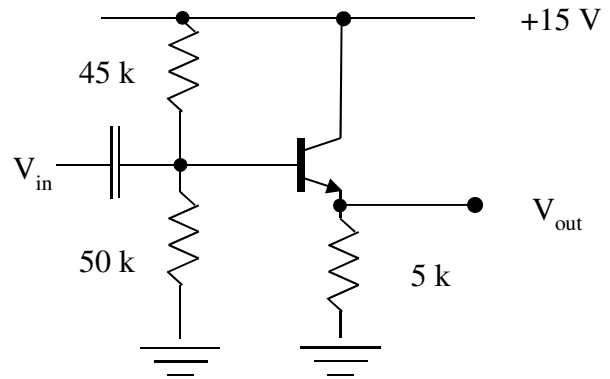1) This is an emitter follower with the base biased quiescently above ground so that a single supply can be used without clipping negative input signals.


- Find the expected quiescent values of V_B , V_E , and V_C .
- Find the expected quiescent values of I_B , I_E , and I_C (hint: start with I_E and assume $\beta=100$).
- Check to make sure that the quiescent I_B is small compared to the quiescent current through the 50k resistor. Why is it important to design the circuit so that this is the case?
- For roughly what range of V_{in} (+ and -) is the output free from clipping?
- Would you need the 45k and 50k resistors if you had a -15V power supply as well as a +15V supply available? Why?



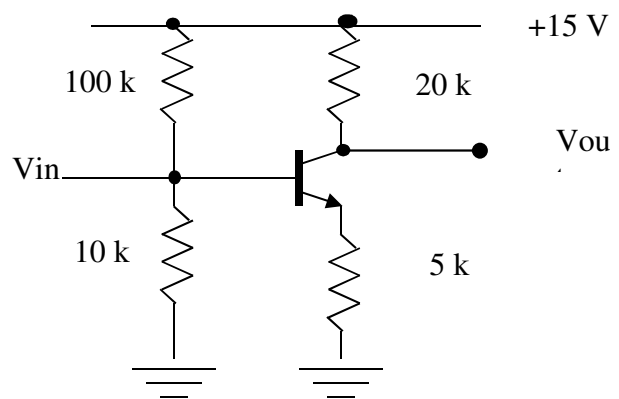- For the common-emitter amplifier at right, what do you expect the quiescent values of V_B , V_E , V_C , I_B , I_E , and I_C to be?
- What are R_{in} , R_{out} , and the voltage gain for the circuit above?
- What is the quiescent value of V_{CE} ? Is this value in the range for which we expect the current gain to be the full $\beta \sim 100$? Explain briefly.



- For the common-emitter amplifier in at right, with $V_{CC}=+15$ V,
 - Choose values for R_C , R_E , R_1 , and R_2 given that the magnitude of the desired voltage amplification is 10, the output resistance should be 10 k, and the quiescent V_{out} should be +6 V. Make sure the 10x rule is obeyed by the transistor and the voltage divider used to bias the base. That is, the transistor (and what follows it) should have a significantly higher impedance than the voltage divider, so that the transistor presents a small "load" to the voltage divider. This implies that the Thévenin resistance of the voltage divider should be at least 10 times smaller than βR_E .
 - Choose the value of C_1 to pass input signals with frequencies above about 500 Hz. Hint: You can treat the circuit as an RC high-pass filter with C_1 as the capacitor and $R_{in}=R_1||R_2||\beta R_E$ as the resistor.

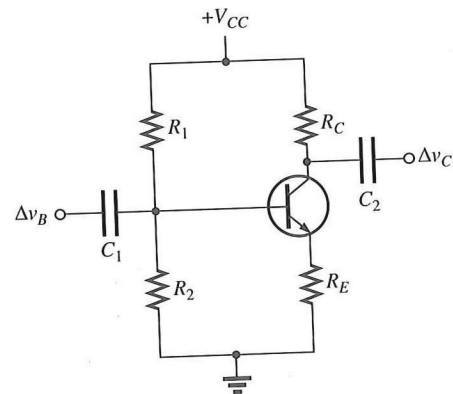

- For a 0.5 V amplitude input sine wave at 10 kHz, give the expected amplitude and frequency of the output signal. Explain briefly. Is the output signal inverted? Is the output signal offset from ground, and if so, by how much?
- What happens if the input signal is a 1.0 V amplitude input sine wave at 10 kHz? Explain your reasoning.

Physics 313 assignment 5 for Tuesday, September 27:

Topics: transistors


Reading questions:

1. For the transistor whose characteristic curves are shown at right,

a) Roughly what is the value of β (or h_{FE}) at V_{CE} of 4 volts, say.

b) If the power rating of the transistor P_{max} is 0.05 W, is there any region of the curves shown for which P_{max} would be exceeded? (Power dissipated by a BJT $\sim V_{CE}I_C$.) Explain. Also, shade in roughly the region where P_{max} is exceeded.

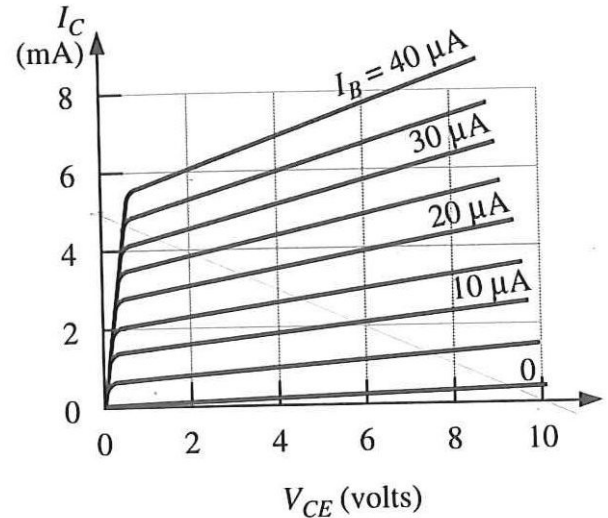2. Setting a voltage at the base of a transistor that's high enough that the base current will be greater than zero for all expected signals is called setting the quiescent point (or "operating point"). What does the word quiescent mean? Give your source. (If you find several definitions, give the one that seems most closely related to its use in this context.)



3. What do the small v 's and i 's used in the textbook mean as distinct from the capital V 's and I 's? (Hint: go back to the first chapter on AC circuits).

4. For the common-emitter amplifier,

- Is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?
- What is the expression for the input impedance?
- What is the expression for the output impedance?

5. For the emitter follower (a.k.a. common collector),


- Is there voltage gain (that is, is v_{out}/v_{in} different from 1)? If so, what does the gain depend on?
- What is the expression for the input impedance? Is this typically a big or a small number?
- What is the expression for the output impedance? Is this typically a big or a small number?

6. Why is it usually useful for a circuit to have a high input impedance and a low output impedance?


Problems: (assume that all transistors are npn silicon, like the 2N3904)

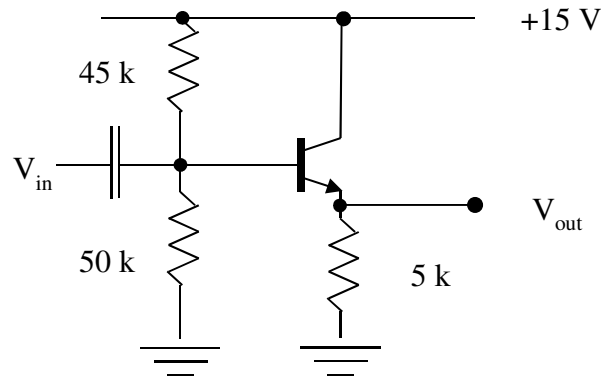1) This is an emitter follower with the base biased quiescently above ground so that a single supply can be used without clipping negative input signals.


- Find the expected quiescent values of V_B , V_E , and V_C .
- Find the expected quiescent values of I_B , I_E , and I_C (hint: start with I_E and assume $\beta=100$).
- Check to make sure that the quiescent I_B is small compared to the quiescent current through the 50k resistor. Why is it important to design the circuit so that this is the case?
- For roughly what range of V_{in} (+ and -) is the output free from clipping?
- Would you need the 45k and 50k resistors if you had a -15V power supply as well as a +15V supply available? Why?



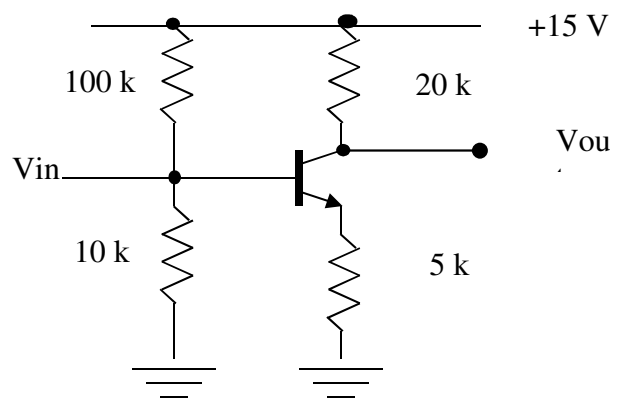- For the common-emitter amplifier at right, what do you expect the quiescent values of V_B , V_E , V_C , I_B , I_E , and I_C to be?
- What are R_{in} , R_{out} , and the voltage gain for the circuit above?
- What is the quiescent value of V_{CE} ? Is this value in the range for which we expect the current gain to be the full $\beta \sim 100$? Explain briefly.



- For the common-emitter amplifier in at right, with $V_{CC}=+15$ V,
 - Choose values for R_C , R_E , R_1 , and R_2 given that the magnitude of the desired voltage amplification is 10, the output resistance should be 10 k, and the quiescent V_{out} should be +6 V. Make sure the 10x rule is obeyed by the transistor and the voltage divider used to bias the base. That is, the transistor (and what follows it) should have a significantly higher impedance than the voltage divider, so that the transistor presents a small "load" to the voltage divider. This implies that the Thévenin resistance of the voltage divider should be at least 10 times smaller than βR_E .
 - Choose the value of C_1 to pass input signals with frequencies above about 500 Hz. Hint: You can treat the circuit as an RC high-pass filter with C_1 as the capacitor and $R_{in}=R_1||R_2||\beta R_E$ as the resistor.

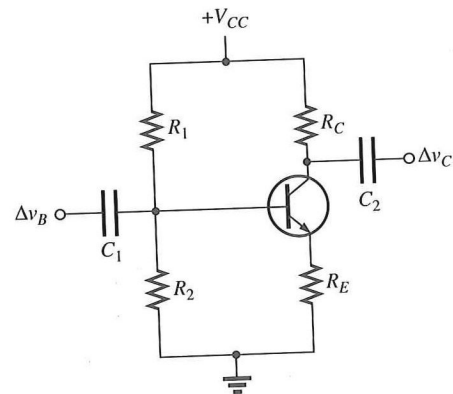

- For a 0.5 V amplitude input sine wave at 10 kHz, give the expected amplitude and frequency of the output signal. Explain briefly. Is the output signal inverted? Is the output signal offset from ground, and if so, by how much?
- What happens if the input signal is a 1.0 V amplitude input sine wave at 10 kHz? Explain your reasoning.

Physics 313 assignment 5 for Tuesday, September 27:

Topics: transistors


Reading questions:

1. For the transistor whose characteristic curves are shown at right,

a) Roughly what is the value of β (or h_{FE}) at V_{CE} of 4 volts, say.

b) If the power rating of the transistor P_{max} is 0.05 W, is there any region of the curves shown for which P_{max} would be exceeded? (Power dissipated by a BJT $\sim V_{CE}I_C$.) Explain. Also, shade in roughly the region where P_{max} is exceeded.

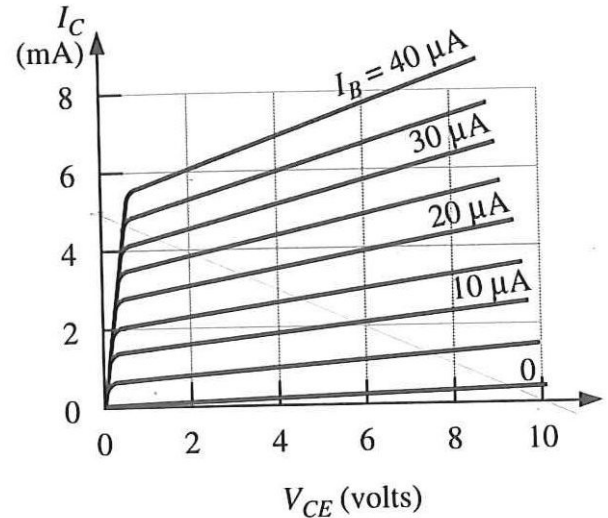2. Setting a voltage at the base of a transistor that's high enough that the base current will be greater than zero for all expected signals is called setting the quiescent point (or "operating point"). What does the word quiescent mean? Give your source. (If you find several definitions, give the one that seems most closely related to its use in this context.)



3. What do the small v 's and i 's used in the textbook mean as distinct from the capital V 's and I 's? (Hint: go back to the first chapter on AC circuits).

4. For the common-emitter amplifier,

- Is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?
- What is the expression for the input impedance?
- What is the expression for the output impedance?

5. For the emitter follower (a.k.a. common collector),


- Is there voltage gain (that is, is v_{out}/v_{in} different from 1)? If so, what does the gain depend on?
- What is the expression for the input impedance? Is this typically a big or a small number?
- What is the expression for the output impedance? Is this typically a big or a small number?

6. Why is it usually useful for a circuit to have a high input impedance and a low output impedance?


Problems: (assume that all transistors are npn silicon, like the 2N3904)

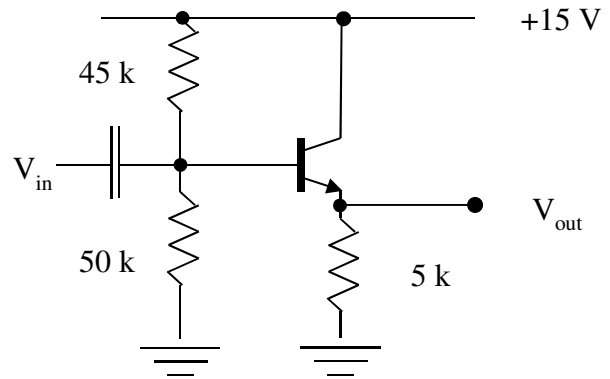1) This is an emitter follower with the base biased quiescently above ground so that a single supply can be used without clipping negative input signals.


- Find the expected quiescent values of V_B , V_E , and V_C .
- Find the expected quiescent values of I_B , I_E , and I_C (hint: start with I_E and assume $\beta=100$).
- Check to make sure that the quiescent I_B is small compared to the quiescent current through the 50k resistor. Why is it important to design the circuit so that this is the case?
- For roughly what range of V_{in} (+ and -) is the output free from clipping?
- Would you need the 45k and 50k resistors if you had a -15V power supply as well as a +15V supply available? Why?



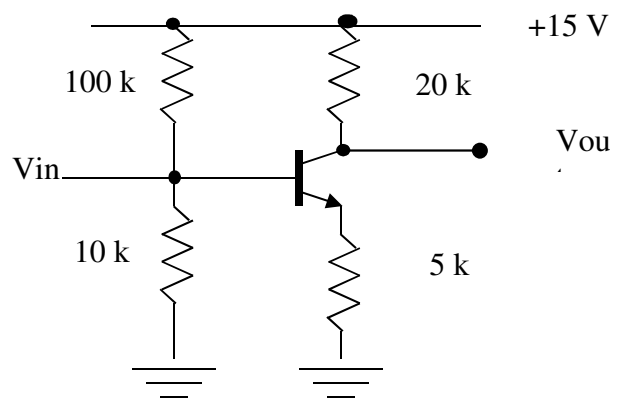- For the common-emitter amplifier at right, what do you expect the quiescent values of V_B , V_E , V_C , I_B , I_E , and I_C to be?
- What are R_{in} , R_{out} , and the voltage gain for the circuit above?
- What is the quiescent value of V_{CE} ? Is this value in the range for which we expect the current gain to be the full $\beta \sim 100$? Explain briefly.



- For the common-emitter amplifier in at right, with $V_{CC}=+15$ V,
 - Choose values for R_C , R_E , R_1 , and R_2 given that the magnitude of the desired voltage amplification is 10, the output resistance should be 10 k, and the quiescent V_{out} should be +6 V. Make sure the 10x rule is obeyed by the transistor and the voltage divider used to bias the base. That is, the transistor (and what follows it) should have a significantly higher impedance than the voltage divider, so that the transistor presents a small "load" to the voltage divider. This implies that the Thévenin resistance of the voltage divider should be at least 10 times smaller than βR_E .
 - Choose the value of C_1 to pass input signals with frequencies above about 500 Hz. Hint: You can treat the circuit as an RC high-pass filter with C_1 as the capacitor and $R_{in}=R_1||R_2||\beta R_E$ as the resistor.

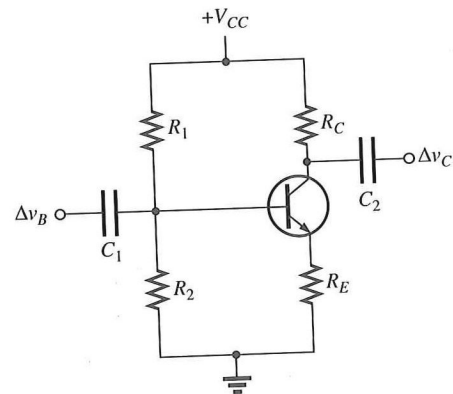

- For a 0.5 V amplitude input sine wave at 10 kHz, give the expected amplitude and frequency of the output signal. Explain briefly. Is the output signal inverted? Is the output signal offset from ground, and if so, by how much?
- What happens if the input signal is a 1.0 V amplitude input sine wave at 10 kHz? Explain your reasoning.

Physics 313 assignment 5 for Tuesday, September 27:

Topics: transistors


Reading questions:

1. For the transistor whose characteristic curves are shown at right,

a) Roughly what is the value of β (or h_{FE}) at V_{CE} of 4 volts, say.

b) If the power rating of the transistor P_{max} is 0.05 W, is there any region of the curves shown for which P_{max} would be exceeded? (Power dissipated by a BJT $\sim V_{CE}I_C$.) Explain. Also, shade in roughly the region where P_{max} is exceeded.

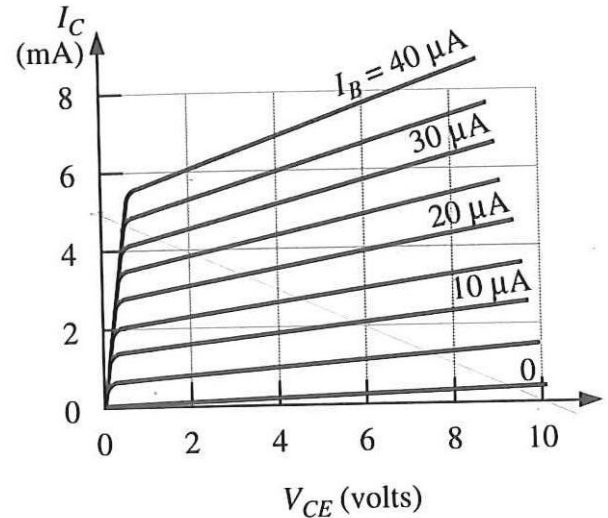2. Setting a voltage at the base of a transistor that's high enough that the base current will be greater than zero for all expected signals is called setting the quiescent point (or "operating point"). What does the word quiescent mean? Give your source. (If you find several definitions, give the one that seems most closely related to its use in this context.)



3. What do the small v 's and i 's used in the textbook mean as distinct from the capital V 's and I 's? (Hint: go back to the first chapter on AC circuits).

4. For the common-emitter amplifier,

- Is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?
- What is the expression for the input impedance?
- What is the expression for the output impedance?

5. For the emitter follower (a.k.a. common collector),


- Is there voltage gain (that is, is v_{out}/v_{in} different from 1)? If so, what does the gain depend on?
- What is the expression for the input impedance? Is this typically a big or a small number?
- What is the expression for the output impedance? Is this typically a big or a small number?

6. Why is it usually useful for a circuit to have a high input impedance and a low output impedance?


Problems: (assume that all transistors are npn silicon, like the 2N3904)

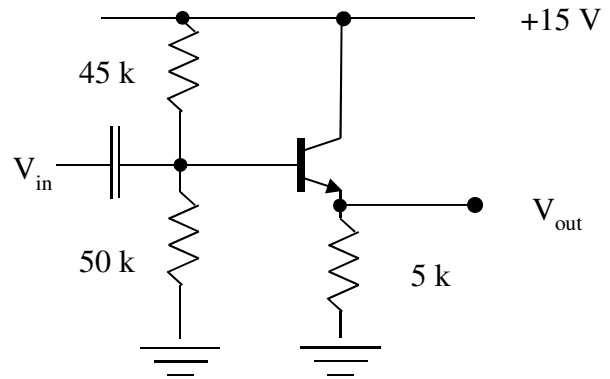1) This is an emitter follower with the base biased quiescently above ground so that a single supply can be used without clipping negative input signals.


- Find the expected quiescent values of V_B , V_E , and V_C .
- Find the expected quiescent values of I_B , I_E , and I_C (hint: start with I_E and assume $\beta=100$).
- Check to make sure that the quiescent I_B is small compared to the quiescent current through the 50k resistor. Why is it important to design the circuit so that this is the case?
- For roughly what range of V_{in} (+ and -) is the output free from clipping?
- Would you need the 45k and 50k resistors if you had a -15V power supply as well as a +15V supply available? Why?



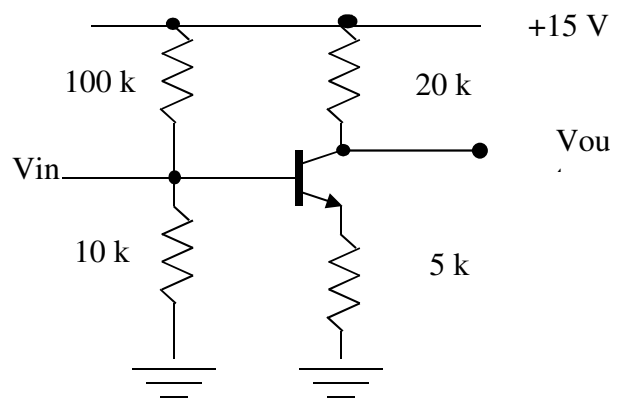- For the common-emitter amplifier at right, what do you expect the quiescent values of V_B , V_E , V_C , I_B , I_E , and I_C to be?
- What are R_{in} , R_{out} , and the voltage gain for the circuit above?
- What is the quiescent value of V_{CE} ? Is this value in the range for which we expect the current gain to be the full $\beta \sim 100$? Explain briefly.



- For the common-emitter amplifier in at right, with $V_{CC}=+15$ V,
 - Choose values for R_C , R_E , R_1 , and R_2 given that the magnitude of the desired voltage amplification is 10, the output resistance should be 10 k, and the quiescent V_{out} should be +6 V. Make sure the 10x rule is obeyed by the transistor and the voltage divider used to bias the base. That is, the transistor (and what follows it) should have a significantly higher impedance than the voltage divider, so that the transistor presents a small "load" to the voltage divider. This implies that the Thévenin resistance of the voltage divider should be at least 10 times smaller than βR_E .
 - Choose the value of C_1 to pass input signals with frequencies above about 500 Hz. Hint: You can treat the circuit as an RC high-pass filter with C_1 as the capacitor and $R_{in}=R_1||R_2||\beta R_E$ as the resistor.

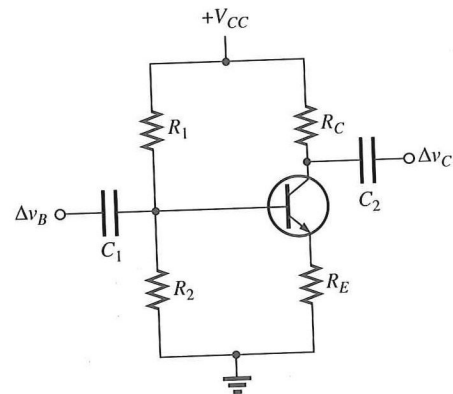

- For a 0.5 V amplitude input sine wave at 10 kHz, give the expected amplitude and frequency of the output signal. Explain briefly. Is the output signal inverted? Is the output signal offset from ground, and if so, by how much?
- What happens if the input signal is a 1.0 V amplitude input sine wave at 10 kHz? Explain your reasoning.

Physics 313 assignment 5 for Tuesday, September 27:

Topics: transistors

Reading questions:

1. For the transistor whose characteristic curves are shown at right,

a) Roughly what is the value of β (or h_{FE}) at V_{CE} of 4 volts, say.

b) If the power rating of the transistor P_{max} is 0.05 W, is there any region of the curves shown for which P_{max} would be exceeded? (Power dissipated by a BJT $\sim V_{CE}I_C$.) Explain. Also, shade in roughly the region where P_{max} is exceeded.

2. Setting a voltage at the base of a transistor that's high enough that the base current will be greater than zero for all expected signals is called setting the quiescent point (or "operating point"). What does the word quiescent mean? Give your source. (If you find several definitions, give the one that seems most closely related to its use in this context.)

3. What do the small v 's and i 's used in the textbook mean as distinct from the capital V 's and I 's? (Hint: go back to the first chapter on AC circuits).


4. For the common-emitter amplifier,

- Is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?
- What is the expression for the input impedance?
- What is the expression for the output impedance?

5. For the emitter follower (a.k.a. common collector),

- Is there voltage gain (that is, is v_{out}/v_{in} different from 1)? If so, what does the gain depend on?
- What is the expression for the input impedance? Is this typically a big or a small number?
- What is the expression for the output impedance? Is this typically a big or a small number?

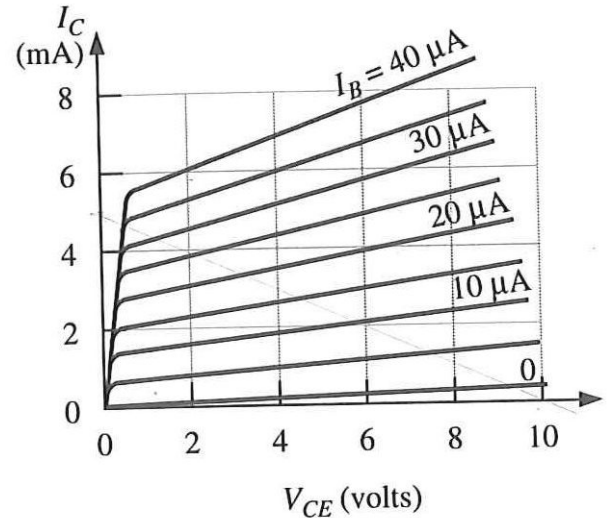
6. Why is it usually useful for a circuit to have a high input impedance and a low output impedance?




Problems: (assume that all transistors are npn silicon, like the 2N3904)

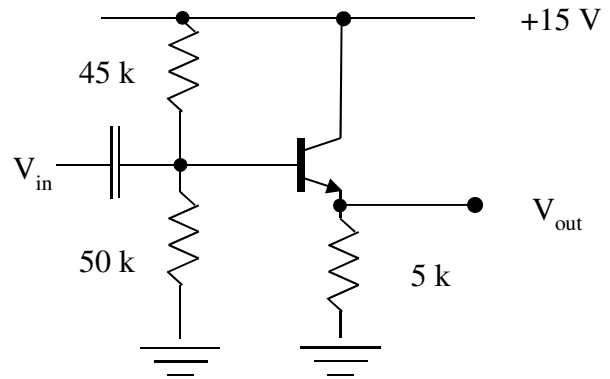1) This is an emitter follower with the base biased quiescently above ground so that a single supply can be used without clipping negative input signals.


- Find the expected quiescent values of V_B , V_E , and V_C .
- Find the expected quiescent values of I_B , I_E , and I_C (hint: start with I_E and assume $\beta=100$).
- Check to make sure that the quiescent I_B is small compared to the quiescent current through the 50k resistor. Why is it important to design the circuit so that this is the case?
- For roughly what range of V_{in} (+ and -) is the output free from clipping?
- Would you need the 45k and 50k resistors if you had a -15V power supply as well as a +15V supply available? Why?



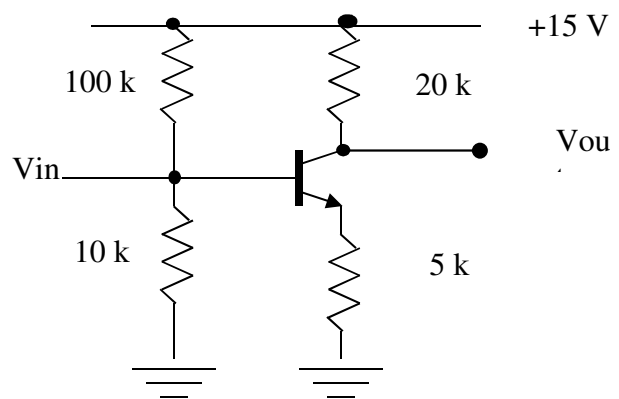- For the common-emitter amplifier at right, what do you expect the quiescent values of V_B , V_E , V_C , I_B , I_E , and I_C to be?
- What are R_{in} , R_{out} , and the voltage gain for the circuit above?
- What is the quiescent value of V_{CE} ? Is this value in the range for which we expect the current gain to be the full $\beta \sim 100$? Explain briefly.



- For the common-emitter amplifier in at right, with $V_{CC}=+15$ V,
 - Choose values for R_C , R_E , R_1 , and R_2 given that the magnitude of the desired voltage amplification is 10, the output resistance should be 10 k, and the quiescent V_{out} should be +6 V. Make sure the 10x rule is obeyed by the transistor and the voltage divider used to bias the base. That is, the transistor (and what follows it) should have a significantly higher impedance than the voltage divider, so that the transistor presents a small "load" to the voltage divider. This implies that the Thévenin resistance of the voltage divider should be at least 10 times smaller than βR_E .
 - Choose the value of C_1 to pass input signals with frequencies above about 500 Hz. Hint: You can treat the circuit as an RC high-pass filter with C_1 as the capacitor and $R_{in}=R_1||R_2||\beta R_E$ as the resistor.

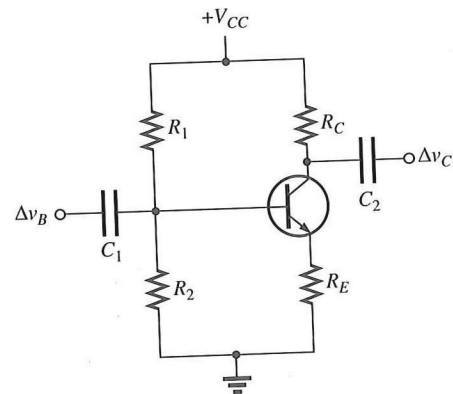

- For a 0.5 V amplitude input sine wave at 10 kHz, give the expected amplitude and frequency of the output signal. Explain briefly. Is the output signal inverted? Is the output signal offset from ground, and if so, by how much?
- What happens if the input signal is a 1.0 V amplitude input sine wave at 10 kHz? Explain your reasoning.

Physics 313 assignment 5 for Tuesday, September 27:

Topics: transistors


Reading questions:

1. For the transistor whose characteristic curves are shown at right,

a) Roughly what is the value of β (or h_{FE}) at V_{CE} of 4 volts, say.

b) If the power rating of the transistor P_{max} is 0.05 W, is there any region of the curves shown for which P_{max} would be exceeded? (Power dissipated by a BJT $\sim V_{CE}I_C$.) Explain. Also, shade in roughly the region where P_{max} is exceeded.

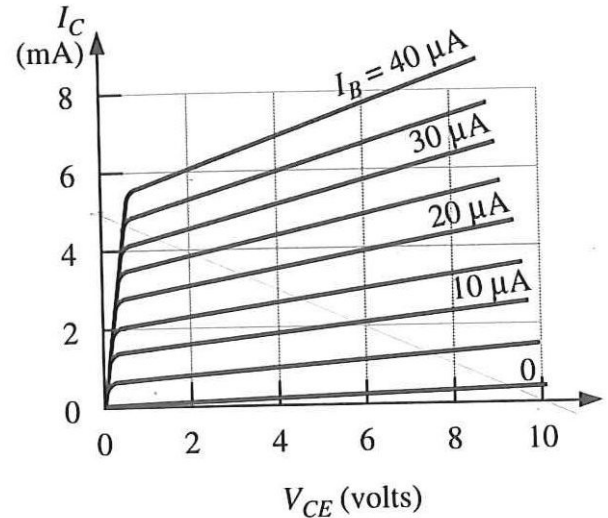2. Setting a voltage at the base of a transistor that's high enough that the base current will be greater than zero for all expected signals is called setting the quiescent point (or "operating point"). What does the word quiescent mean? Give your source. (If you find several definitions, give the one that seems most closely related to its use in this context.)



3. What do the small v 's and i 's used in the textbook mean as distinct from the capital V 's and I 's? (Hint: go back to the first chapter on AC circuits).

4. For the common-emitter amplifier,

- Is there voltage gain (that is, is v_{out}/v_{in} much different from 1)? If so, what does the gain depend on?
- If the voltage at the base rises by 0.1 V, what does the voltage at the emitter rise by?
- Is the output signal inverted with respect to the input signal?
- What is the expression for the input impedance?
- What is the expression for the output impedance?

5. For the emitter follower (a.k.a. common collector),


- Is there voltage gain (that is, is v_{out}/v_{in} different from 1)? If so, what does the gain depend on?
- What is the expression for the input impedance? Is this typically a big or a small number?
- What is the expression for the output impedance? Is this typically a big or a small number?

6. Why is it usually useful for a circuit to have a high input impedance and a low output impedance?


Problems: (assume that all transistors are npn silicon, like the 2N3904)

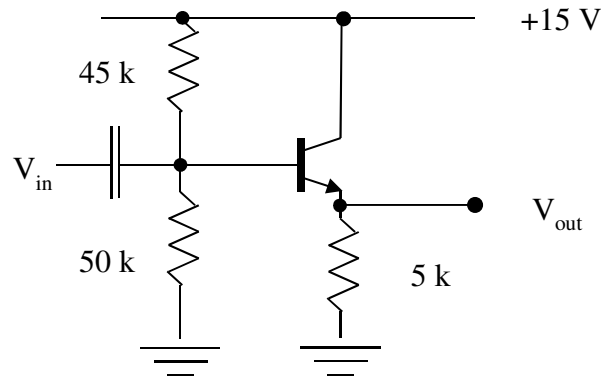1) This is an emitter follower with the base biased quiescently above ground so that a single supply can be used without clipping negative input signals.


- Find the expected quiescent values of V_B , V_E , and V_C .
- Find the expected quiescent values of I_B , I_E , and I_C (hint: start with I_E and assume $\beta=100$).
- Check to make sure that the quiescent I_B is small compared to the quiescent current through the 50k resistor. Why is it important to design the circuit so that this is the case?
- For roughly what range of V_{in} (+ and -) is the output free from clipping?
- Would you need the 45k and 50k resistors if you had a -15V power supply as well as a +15V supply available? Why?



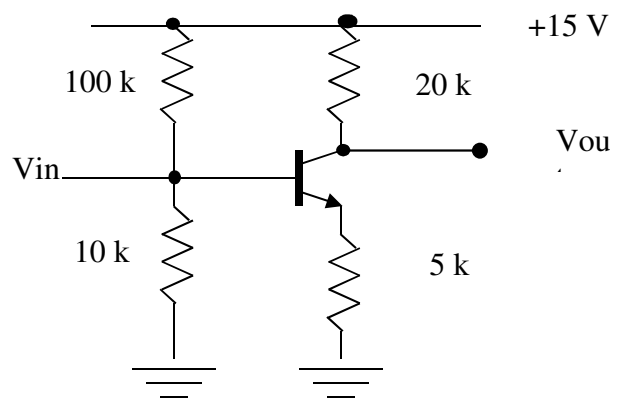- For the common-emitter amplifier at right, what do you expect the quiescent values of V_B , V_E , V_C , I_B , I_E , and I_C to be?
- What are R_{in} , R_{out} , and the voltage gain for the circuit above?
- What is the quiescent value of V_{CE} ? Is this value in the range for which we expect the current gain to be the full $\beta \sim 100$? Explain briefly.



- For the common-emitter amplifier in at right, with $V_{CC}=+15$ V,
 - Choose values for R_C , R_E , R_1 , and R_2 given that the magnitude of the desired voltage amplification is 10, the output resistance should be 10 k, and the quiescent V_{out} should be +6 V. Make sure the 10x rule is obeyed by the transistor and the voltage divider used to bias the base. That is, the transistor (and what follows it) should have a significantly higher impedance than the voltage divider, so that the transistor presents a small "load" to the voltage divider. This implies that the Thévenin resistance of the voltage divider should be at least 10 times smaller than βR_E .
 - Choose the value of C_1 to pass input signals with frequencies above about 500 Hz. Hint: You can treat the circuit as an RC high-pass filter with C_1 as the capacitor and $R_{in}=R_1||R_2||\beta R_E$ as the resistor.

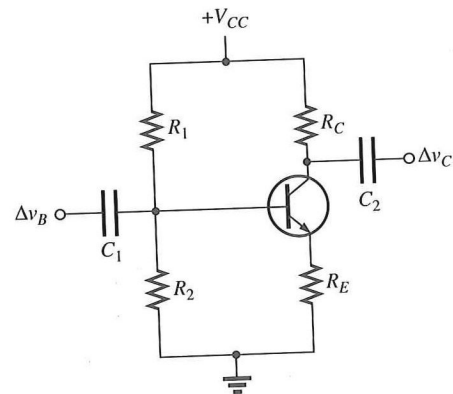

- For a 0.5 V amplitude input sine wave at 10 kHz, give the expected amplitude and frequency of the output signal. Explain briefly. Is the output signal inverted? Is the output signal offset from ground, and if so, by how much?
- What happens if the input signal is a 1.0 V amplitude input sine wave at 10 kHz? Explain your reasoning.